

Design Project

Student Name

İsmet Mert ŞEN

210702011

Ahmad Zameer NAZARI

220702706

Name of Lecturers

Doktor Öğretim Üyesi Kutlu KARAYAHŞI

Date:24.11.24

EEE 3003 Electromechanical Energy Conversion


→ In a transformer, its excitation branch components, series impedances, and in addition various losses voltage regulation and efficiency are very essential quantities that describe a transformer

All of these quantities can be determined from a small set of initial data about the transformer and a few experimental tests, namely the open & short-circuit test.


→ Suppose the given transformer is a 15kVA, 2300/230V transformer, and its open and short circuit test results are:
 open circuit test → $V_{oc} = 230V$, $I_{oc} = 2.1A$, $P_{oc} = 50W$
 short circuit test → $V_{sc} = 47V$, $I_{sc} = 6.0A$, $P_{sc} = 160W$

→ The given transformer is a step-down one with rated primary voltage, $V_1 = 2300V$ & secondary, $V_2 = 230V$ and turns ratio, $a = 10$

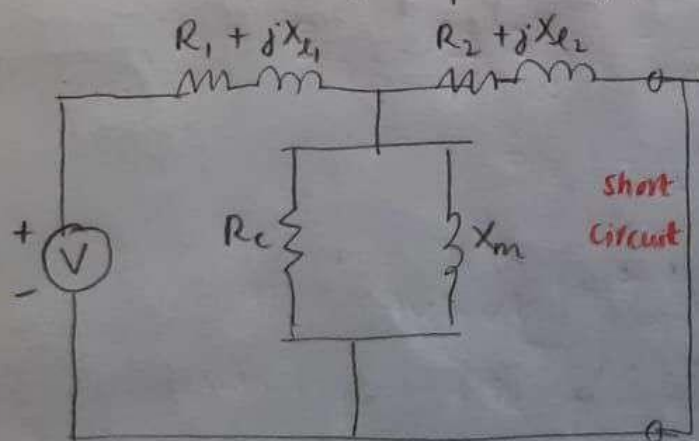→ Since in short circuit test, the low voltage (here, secondary) side is short circuited and measurements are taken on the high-voltage (primary) side, we have the schematic diagram



HV primary ; LV secondary

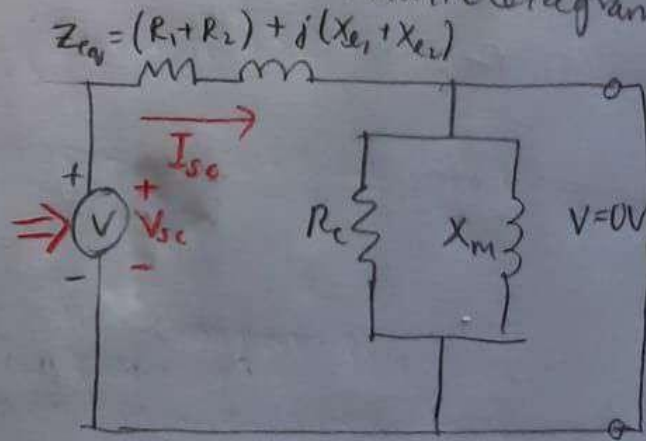

when Z_{eq} referred to primary

now the series equivalent impedance, Z_{eq} can be found:-

$$\text{power factor} = PF = \cos \theta = \frac{P_{sc}}{V_{sc} I_{sc}} = \frac{160W}{(47V)(6A)} = 0.567$$

$$\text{then:- } \theta = \cos^{-1}(PF) = 55.4^\circ$$

$$\text{then:- } Z_{eq} = \frac{V_{sc}}{I_{sc} \angle \theta} = \frac{47V \angle 55.4^\circ}{6A}$$



$$Z_{eq} = 7.83 \angle 55.4^\circ \Omega$$

$$\text{OR } R_{eq} = \frac{P_{sc}}{I_{sc}^2} = |Z_{eq}| \cos \theta = 4.45 \Omega$$

$$\text{and } X_{eq} = \sqrt{|Z_{eq}|^2 - R_{eq}^2} = |Z_{eq}| \sin \theta = 6.45 \Omega$$

$$\text{hence:- } Z_{eq} = R_{eq} + jX_{eq} = 4.45 + j6.45 \Omega$$

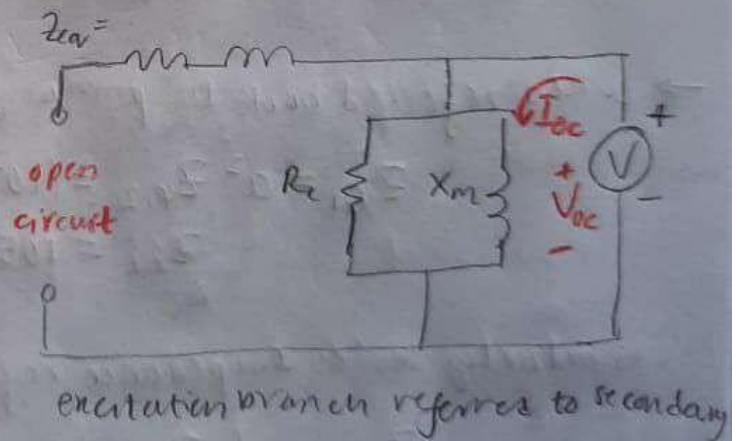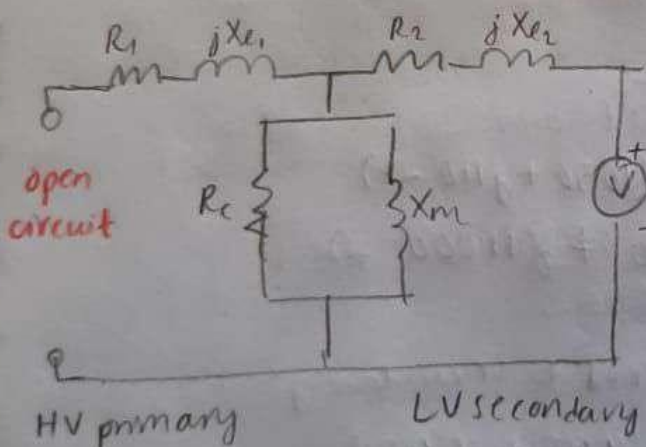→ In an open circuit test, the HV side (primary) is open-circuited and measurements are taken on the LV (secondary) side, so:-



now the excitation branch impedance, Z_ϕ can be found:-

$$\text{power factor} = PF = \cos \theta = \frac{P_{oc}}{V_{oc} I_{oc}} = \frac{50W}{230V \cdot 2.1A} = 0.103$$

$$\theta = \cos^{-1}(PF) = 84.1^\circ$$

the excitation branch impedance corresponds to the parallel admittance, Y_ϕ , so:-

$$Y_\phi = \frac{I_{oc} \angle -\theta}{V_{oc}} = \frac{2.3A \angle -84.1^\circ}{230V}$$

$$Y_\phi = 0.00913 \angle -84.1^\circ S$$

where conductance:- $G_\phi = |Y_\phi| \cos(-84.1^\circ) = 0.00954 S$

and susceptance:- $B_\phi = |Y_\phi| \sin(-84.1^\circ) = -0.00908 S$

then:- $Y_\phi = 0.00954 - j0.00908 S$

then:- resistance:- $R_c = \frac{1}{G_\phi} = 1050 \Omega$

and reactance:- $X_m = \frac{1}{|B_\phi|} = 110 \Omega$

and impedance:- $Z_\phi = R_c + jX_m = 1050 + j110 \Omega$

→ when referred back to primary:-

$$Z_{\phi,1} = a^2 Z_{\phi,2} = (10^2)(1050 + j110 \Omega)$$



$$Z_{\phi,1} = 10500 + j11000 \Omega$$

similarly series impedance referred to secondary:-

$$Z_{eq,2} = \frac{1}{a^2} Z_{eq,1} = \frac{1}{10^2} (4.45 + j6.45)$$

$$Z_{eq,2} = 0.0445 + j0.0645 \Omega$$

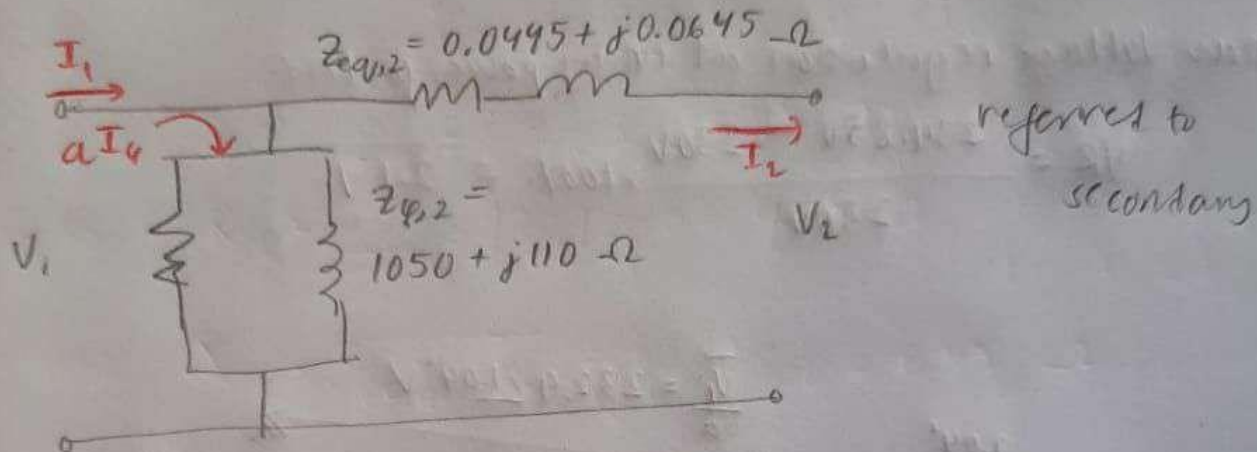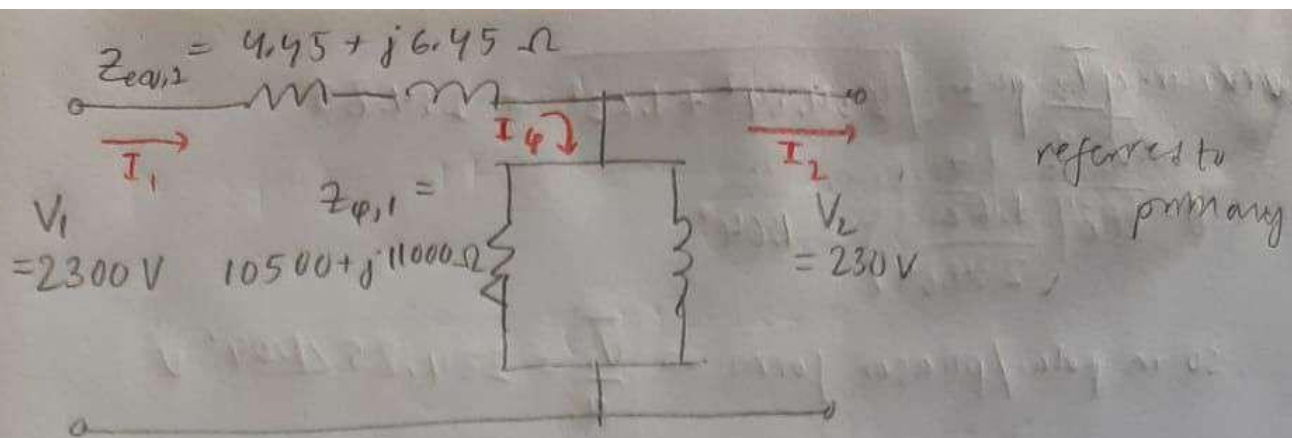then schematic symbols when components are referred to primary and secondary, respectively



→ The voltage regulation of a transformer is defined as

$$VR = \frac{V_{2,ne} - V_{2,fl}}{V_{2,fl}} \times 100\% =$$

where at no load, secondary voltage $\rightarrow V_{2,ne} = \frac{V_1}{a}$

which can be determined from the transformer phasor diagram

$$\frac{\vec{V}_1}{a} = \vec{V}_2 + R_{eq} \vec{I}_2 + jX_{eq} \vec{I}_2$$

but first $|I_2| = \text{full load current} = \frac{S_{rated}}{V_{2,rated}} = \frac{15000 \text{ VA}}{230 \text{ V}} = 65.2 \text{ A}$

assuming unity power factor $\rightarrow I_2 = |I_2| \angle 0^\circ = 65.2 \angle 0^\circ \text{ A}$

$$I_2 = 65.2 \angle 0^\circ = 65.2 \text{ A}$$

then $\frac{\vec{V}_1}{a} = 230 \angle 0^\circ \text{ V} + (0.0445 \Omega)(65.2 \angle 0^\circ \text{ A}) + j(0.0645 \Omega)(65.2 \angle 0^\circ \text{ A})$

$$= 230 \angle 0^\circ \text{ V} + 2.9 \angle 0^\circ \text{ V} + j4.21 \angle 0^\circ \text{ V}$$

$$\frac{\vec{V}_1}{a} = 232.9 + j4.21$$


where $|\frac{\vec{V}_2}{a}| = \sqrt{234.84^2 + 1.62^2} = 234.85$

$\theta = \tan^{-1}\left(\frac{1.62}{234.84}\right) = 1.04^\circ$

so in polar/phasor form $\rightarrow \frac{\vec{V}_2}{a} = 234.85 \angle 1.04^\circ \text{ V}$

now voltage regulation at unity power factor.

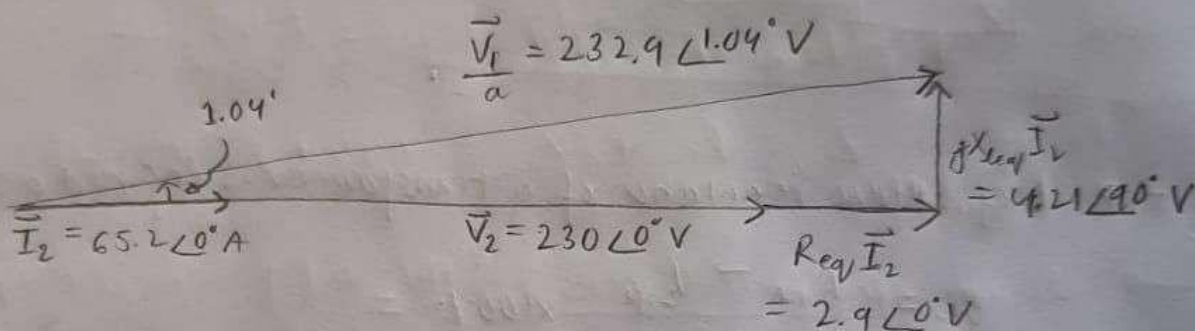$VR = \frac{234.85 \text{ V} - 230 \text{ V}}{230 \text{ V}} \times 100\% = 2.1\%$



→ the transformer classes can be determined:-

copper loss $= P_{cu} = I_1^2 R_{eq} = (65.2)^2 (0.0445 \Omega) = 189 \text{ W}$

core losses $= P_{core} = \frac{(V_{2,nc})^2}{R_c} = \frac{(234.85 \text{ V})^2}{1050 \Omega} = 52.5 \text{ W}$
 = hysteresis & eddy

→ transformer efficiency is:-

power output $= P_{out} = P_2 = V_2 I_2 \cos \theta = S_{2, rated} = 15,000 \text{ W}$

power input $= P_{in} = P_{out} + P_{losses} = P_2 + P_{cu} + P_{core}$
 $= 15,000 \text{ W} + 189 \text{ W} + 52.5 \text{ W} = 15241.5 \text{ W}$

then efficiency $= \eta = \frac{P_{out}}{P_{in}} \times 100\% = \frac{P_2}{P_1 + P_{cu} + P_{core}} \times 100\%$

$\eta = 98.41\%$